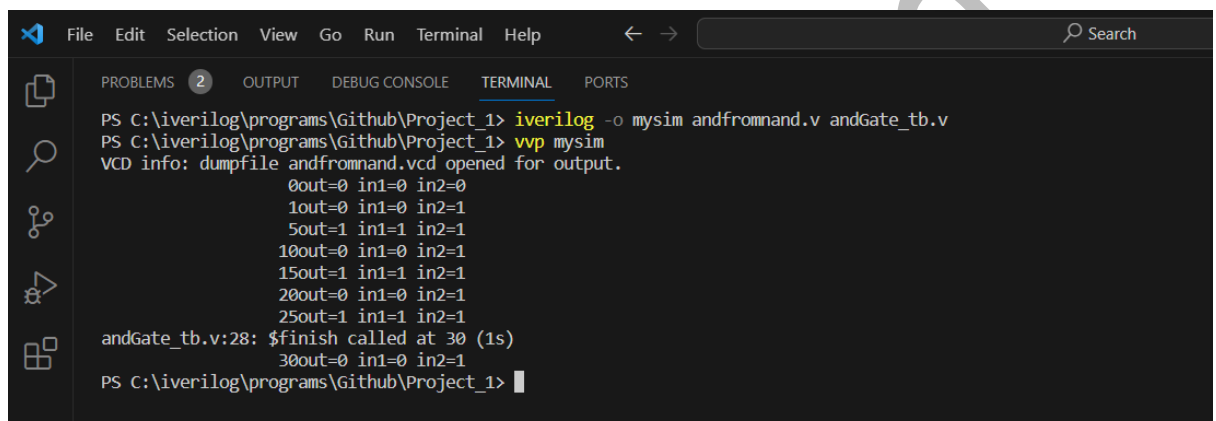


# PROJECT-2


## OUTPUTS

Developed by: Aashi Srivastava National Institute of Technology, Warangal
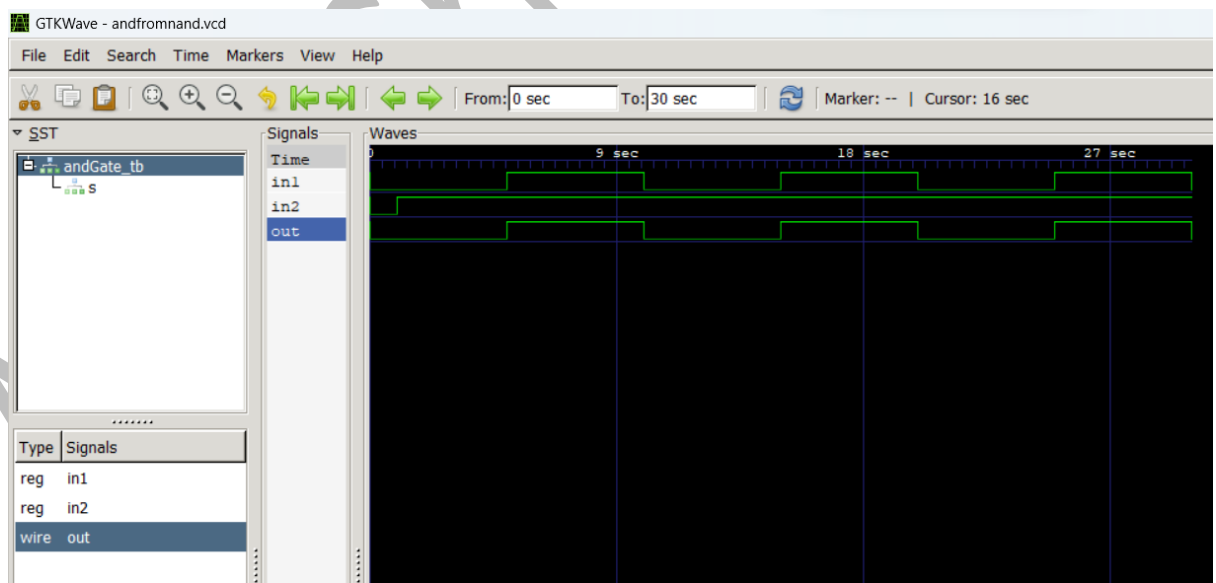
### 1. AND FROM NAND




```
PS C:\iverilog\programs\Github\Project_1> iverilog -o mysim andfromnand.v andGate_tb.v
PS C:\iverilog\programs\Github\Project_1> vvp mysim
VCD info: dumpfile andfromnand.vcd opened for output.
    0out=0 in1=0 in2=0
    1out=0 in1=0 in2=1
    5out=1 in1=1 in2=1
   10out=0 in1=0 in2=1
   15out=1 in1=1 in2=1
   20out=0 in1=0 in2=1
   25out=1 in1=1 in2=1
andGate_tb.v:28: $finish called at 30 (1s)
   30out=0 in1=0 in2=1
PS C:\iverilog\programs\Github\Project_1>
```



 
## 2. NOR FROM NAND

```
PS C:\iverilog\programs\Github\Project_1> iverilog -o mysim norfromnand.v norGate_tb.v
PS C:\iverilog\programs\Github\Project_1> vvp mysim
VCD info: dumpfile norfromnand.vcd opened for output.
    0out=1 in1=0 in2=0
    1out=0 in1=0 in2=1
    5out=0 in1=1 in2=1
   10out=0 in1=0 in2=1
   15out=0 in1=1 in2=1
   20out=0 in1=0 in2=1
   25out=0 in1=1 in2=1
norGate_tb.v:28: $finish called at 30 (1s)
   30out=0 in1=0 in2=1
PS C:\iverilog\programs\Github\Project_1>
```



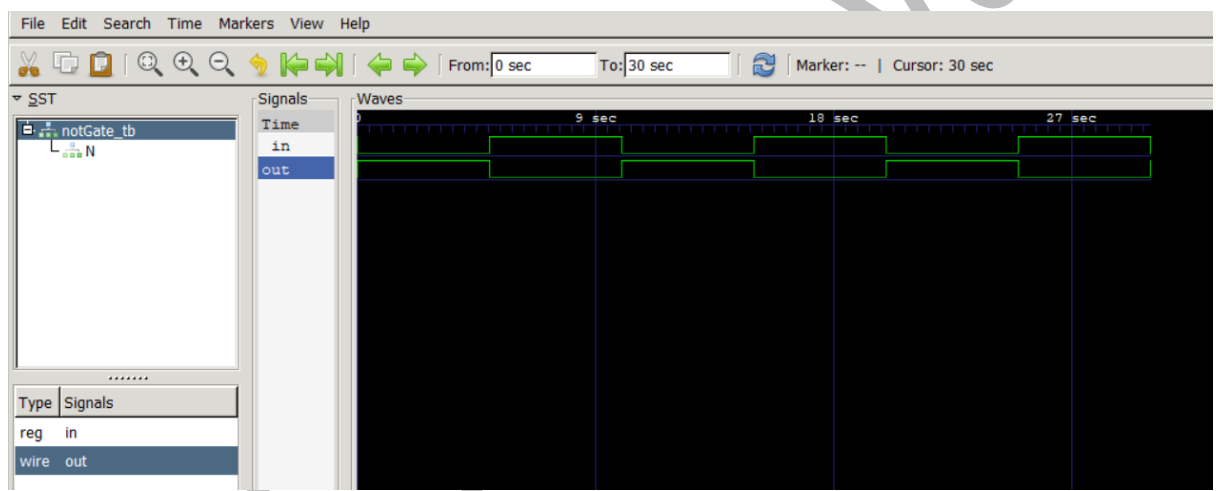
### 3. NOT FROM NAND

```
PS C:\iverilog\programs\Github\Project_1> iverilog -o mysim notfromnand.v notGate_tb.v
PS C:\iverilog\programs\Github\Project_1> vvp mysim
VCD info: dumpfile notfromnand.vcd opened for output.
      0out=1 in=0
      5out=0 in=1
     10out=1 in=0
     15out=0 in=1
     20out=1 in=0
     25out=0 in=1
notGate_tb.v:26: $finish called at 30 (1s)
     30out=1 in=0
PS C:\iverilog\programs\Github\Project_1> █
```



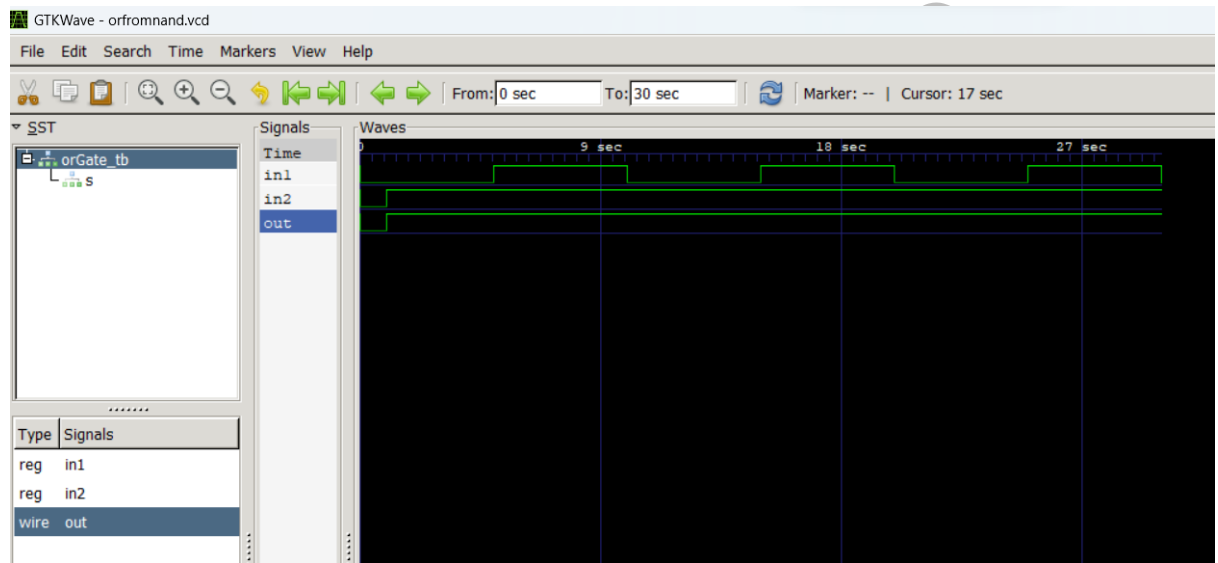
#### 4. OR FROM NAND

```
1 Error(s) during elaboration.  
PS C:\iverilog\programs\Github\Project_1> iverilog -o mysim orfromnand.v orGate_tb.v  
PS C:\iverilog\programs\Github\Project_1> vvp mysim  
VCD info: dumpfile orfromnand.vcd opened for output.  
0out=0 in1=0 in2=0  
1out=1 in1=0 in2=1  
5out=1 in1=1 in2=1  
10out=1 in1=0 in2=1  
15out=1 in1=1 in2=1  
20out=1 in1=0 in2=1  
25out=1 in1=1 in2=1  
orGate_tb.v:28: $finish called at 30 (1s)
```



## 5. XNOR FROM NAND

```
[0] start time.  
PS C:\iverilog\programs\Github\Project_1> iverilog -o mysim xnorfromnand.v xnorGate_tb.v  
PS C:\iverilog\programs\Github\Project_1> vvp mysim  
VCD info: dumpfile xnorfromnand.vcd opened for output.  
      0out=1 in1=0 in2=0  
      1out=0 in1=0 in2=1  
      5out=1 in1=1 in2=1  
     10out=0 in1=0 in2=1  
     15out=1 in1=1 in2=1  
     20out=0 in1=0 in2=1  
     25out=1 in1=1 in2=1  
xnorGate_tb.v:27: $finish called at 30 (1s)  
     30out=0 in1=0 in2=1  
PS C:\iverilog\programs\Github\Project_1> |
```

 

## 6. XOR FROM NAND

```
PS C:\iverilog\programs\Github\Project_1> iverilog -o mysim xorfornand.v xorGate_tb.v
PS C:\iverilog\programs\Github\Project_1> vvp mysim
VCD info: dumpfile xorfornand.vcd opened for output.
      0out=0 in1=0 in2=0
      1out=1 in1=0 in2=1
      5out=0 in1=1 in2=1
     10out=1 in1=0 in2=1
     15out=0 in1=1 in2=1
     20out=1 in1=0 in2=1
     25out=0 in1=1 in2=1
xorGate_tb.v:28: $finish called at 30 (1s)
     30out=1 in1=0 in2=1
PS C:\iverilog\programs\Github\Project_1> |
```

